



Potential difference of one Cell = 1.5V Electrodynamics

CH # 12 "Current Electricity"

Dated: - 11 OCT, 2017

Electric Current :-

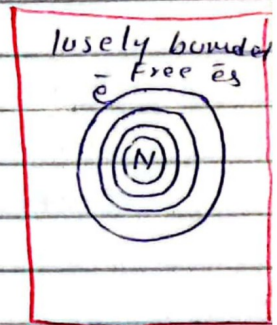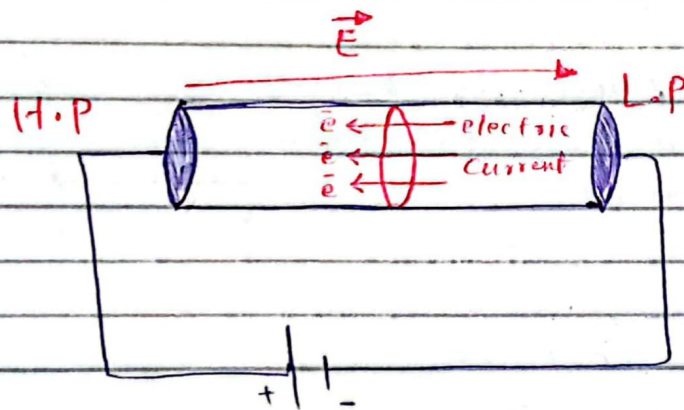The rate of flow of charges passing through any cross-sectional area of a conductor is called electric current.



* Because of random motion of e^- , electric field inside the conductor is zero.


$$I = \frac{\Delta Q}{\Delta t}$$

UNIT :-

$$1A = \frac{1C}{1Sec}$$

$$1e^- = \frac{1.6 \times 10^{-19} C}{1.6 \times 10^{-19}}$$
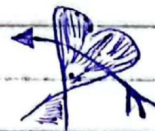
$$1C = \frac{1}{1.6 \times 10^{-19} e^-} \Rightarrow 1C = 6.25 \times 10^{18} e^-$$





* In Metals Current is due to flow of e^- .

* Semi-conductors $\rightarrow e^-$ and holes.

* Solutions \rightarrow opposite Ions

(i) Conventional Current :- A Current which flows from high potential to low potential...

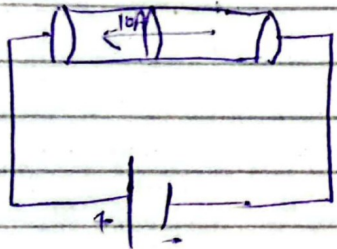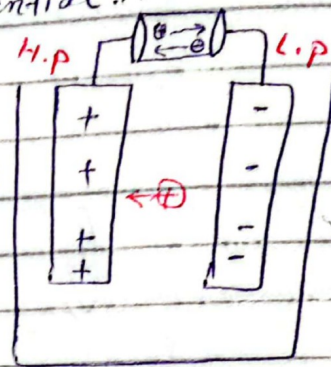(ii) Electronic Current :- A Current which is due to the flow of negatively charged electrons is called electronic current.




* Basically e^- moves from one plate to another and neutralize $+$.
* Positive charges do not move at convention... but it is

A Current which is equal to electronic current in magnitude but is in opposite direction is called conventional current.

Drift of e^- in Metallic conductors:

push on e^- by external electric field.

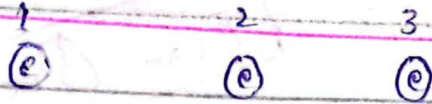Thermal velocity: without external \vec{E} field



Drift velocity:-

The average velocity gained by e^- with which they get drifted under the influence of external electric field.

V_d : Drift velocity...


$$V_{\text{effective}} \approx C \quad V_d \approx 10^6 \text{ m/s}$$

12 OCT, 2017

Electroencephalography (E.E.G).

A neurological ^{test} activity by which we measure electrical activity

of brain by using a monitor.

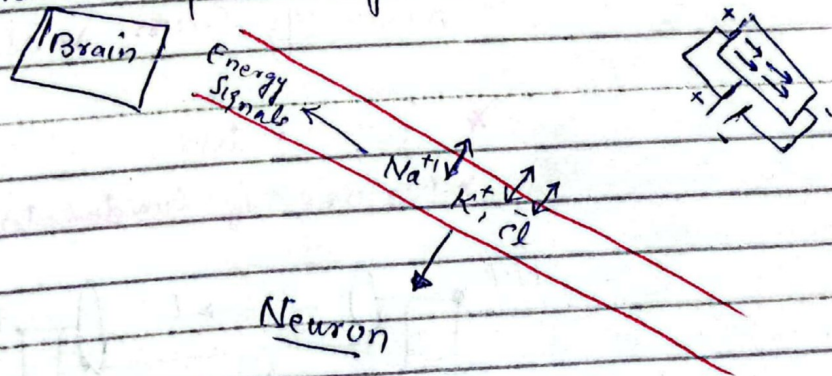

Exam Que

Ohm's Law:-


This Law States that "the magnitude of Current (I) passing through a conductor is directly proportional to the magnitude of potential difference (V) across its two ends, provided the physical state of the conductor remains constant".

* Length

* Area of Cross Section

* Temperature.

* Nature of conductor

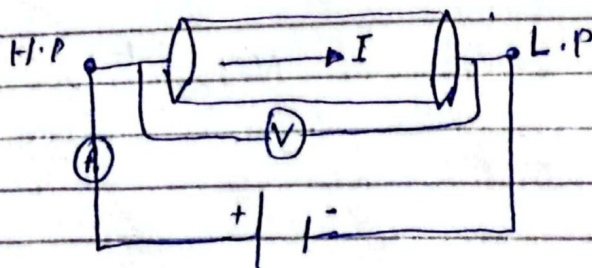

$$I \propto V$$


$V = IS$ Independent
 $I = \frac{V}{R}$ dependent.

$$I = kV$$

$$k = \frac{1}{R}$$

$$I = \frac{V}{R}$$

$$V = IR$$

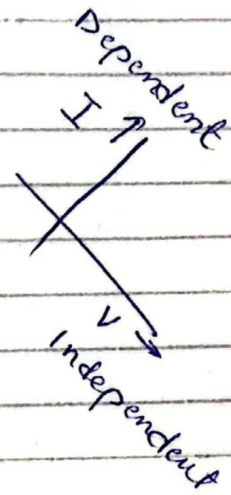

Ohm's Law relate Current and
Voltage through resistor...


$$R = \frac{V}{I}$$

$$1\Omega = \frac{1V}{1A}$$

Resistance:-

The opposition offered by
a conductor to the flow of
~~charge~~ Current is called Resistance.
Current

V	I	$R = \frac{V}{I}$
2	1	2
4	2	2
6	3	2
8	4	2
10	5	2
12	6	2

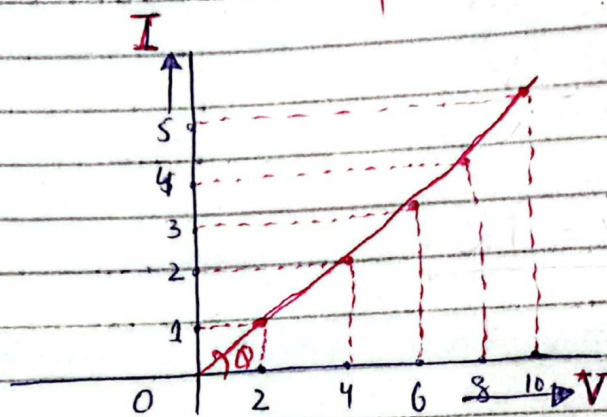

* Any conductor which satisfy ohm law called ohmic conductor.

* For same straight line slope remains constant. $\theta = \frac{y}{x}$

$$\text{slope} = \tan \theta$$

$$K = \frac{I}{V}$$

$$\therefore V = IR$$

$$R = \frac{V}{I}$$

$$\frac{I}{V} = \frac{1}{R}$$

$$K = \frac{1}{R}$$

* The slope = Shows reciprocal of resistance.

* 1 $(K = \frac{1}{R})$

* The reciprocal of slope gives us Resistance of the conductor.


$$\text{i.e. } \frac{1}{\text{slope}} = R$$

MCO:- The resistance of conductor resemble to the

(a) Mass of body.


$$F = ma$$

$$V = IR$$

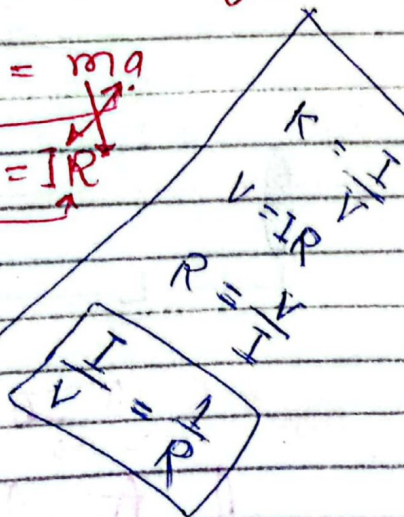

$a = \frac{F}{m}$
 mass is opposition to acceleration.
 $R = \frac{V}{I}$ opposition to current.

Filament of a bulb:-

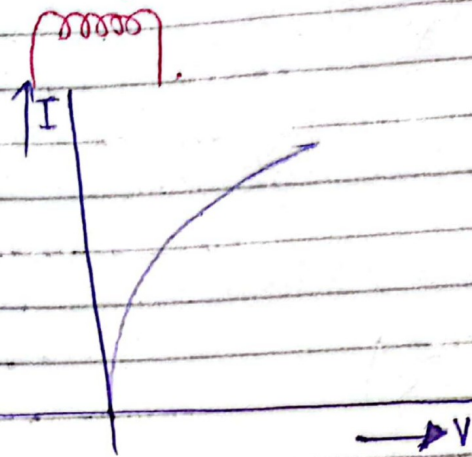

* $I = \frac{V}{R}$

When R increases in filament,

then I do not increases, ~~it~~ is decreasing.

* So, Filament of a bulb is non-ohmic conductor.




13 OCT, 2017

Factors Upon which Resistance depends:-

(i) Dimensions:-

$R \propto L$ — (i)

$R \propto \frac{1}{A}$ — (ii)

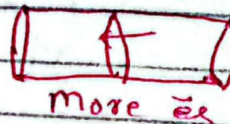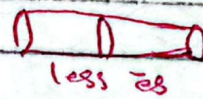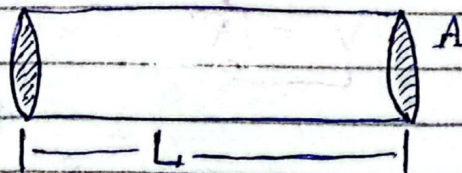

Combining the relations:

$$R \propto \frac{L}{A}$$

$$R = \frac{\rho L}{A}$$

ρ = Specific Resistance, or
Resistivity of the conductor
Specific Resistivity.

$$\rho = \frac{RA}{L}$$

Resistance

opposition offered
by conductor.

$$R = \frac{V}{I}$$

* Unit is Ω (ohm)

Resistivity

The Resistance of
a unit area of
cross section of a
wire per unit length.

$$\rho = \frac{RA}{L}$$

$$\rho = \frac{\Omega \cdot m}{\frac{m^2}{m}} = \Omega \cdot m$$


ρ depends upon:

* Temperature

* Nature of the conductor

Resistor:-

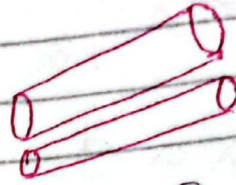A conductor use
for Resistance conductor.



③ → Necessary



Variable Resistor

$$\rho = \frac{RA}{L} \rightarrow \begin{array}{l} A \text{ more} \\ R \text{ - less} \\ L \text{ - Same} \end{array} \quad \rho \text{ - constant}$$

Conductance:- (G)

The Reciprocal of
Resistance of a conductor
is called Conductance.

Unit:-

$$G = \frac{1}{R}$$

$$= \frac{1}{\Omega}$$

$$= \Omega^{-1}$$

= Siemens → Name of Scientist...

$$\boxed{G = S}$$

(Sigma)

Conductivity:- (σ)

The Reciprocal of Resistivity
of a conductor is called
conductivity.

$$\sigma = \frac{1}{\rho}$$

$$\sigma = \frac{1}{\Omega \cdot m}$$

$$\sigma = (\Omega \cdot m)^{-1}$$

$$\sigma = \Omega^{-1} \cdot m^{-1}$$

$$\sigma = \text{mho} \cdot m^{-1}$$

ohm = mho

$$\sigma = \frac{\text{mho}}{m}$$

Conductivity

$$\sigma = \frac{S}{m}$$

Semen = Ω^{-1}

2. Variation of Resistance with temperature :-

$$R_2 - R_1 \propto R_1 \text{ --- (i)}$$


$$R_2 - R_1 \propto \Delta T \text{ --- (ii)}$$

$$R_2 - R_1 \propto R_1 \Delta T$$

$$R_2 - R_1 = \alpha R_1 \Delta T \text{ --- (iii)}$$

$$R_2 = R_1 + \alpha R_1 \Delta T$$

$$R_2 = R_1 (1 + \alpha \Delta T)$$

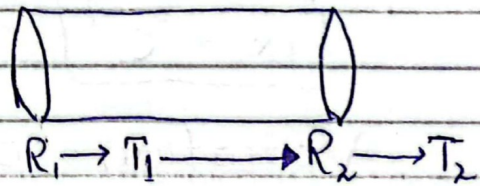

$$3 \Rightarrow \Delta R = \alpha R_1 \Delta T$$

$$\alpha = \frac{\Delta R}{R_1 \Delta T}$$

Temperature coefficient of Resistance.


α = change in Resistance per degree rise in temperature to the initial resistance.

$$\alpha = \frac{\Delta R}{R \cdot K}$$

$$\alpha = K^{-1}$$

$$\alpha = ^\circ C^{-1}$$

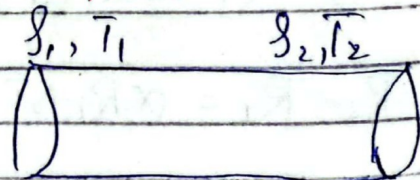Variation of Resistivity with temperature:-



$$\rho = \frac{RA}{L}$$

$$R_2 - R_1 \propto R_1 \quad \text{--- (i)}$$

$$R_2 - R_1 \propto \Delta T \quad \text{--- (ii)}$$

$$R_2 - R_1 \propto R_1 \Delta T$$

$$R_2 - R_1 = \alpha R_1 \Delta T \quad \text{--- (iii)}$$

$$R_2 = R_1 + \alpha R_1 \Delta T$$

$$R_2 = R_1 (1 + \alpha \Delta T) \quad \text{--- (iv)}$$

$$\textcircled{3} \Rightarrow \Delta R = \alpha R_1 \Delta T$$

$$\boxed{\alpha = \frac{\Delta R}{R_1 \Delta T}}$$

Temp coefficient of Resistivity..

Unit is Same as:

$$\boxed{\begin{array}{l} \alpha = K^{-1} \\ \alpha = \text{ }^\circ\text{C}^{-1} \end{array}}$$

: 14 Oct, 2017:

Wire Wound Resistors:-


We use alloys in Resistors.

1. Manganin (Manganese, Copper, Nickel)
2. Constantan (Copper, Nickel)
50%, 50%
3. Eureka (Copper, Nickel)

Wires are made from these alloys, which are then used as Resistors.

Ⓐ Rheostat:- "Variable Resistor"


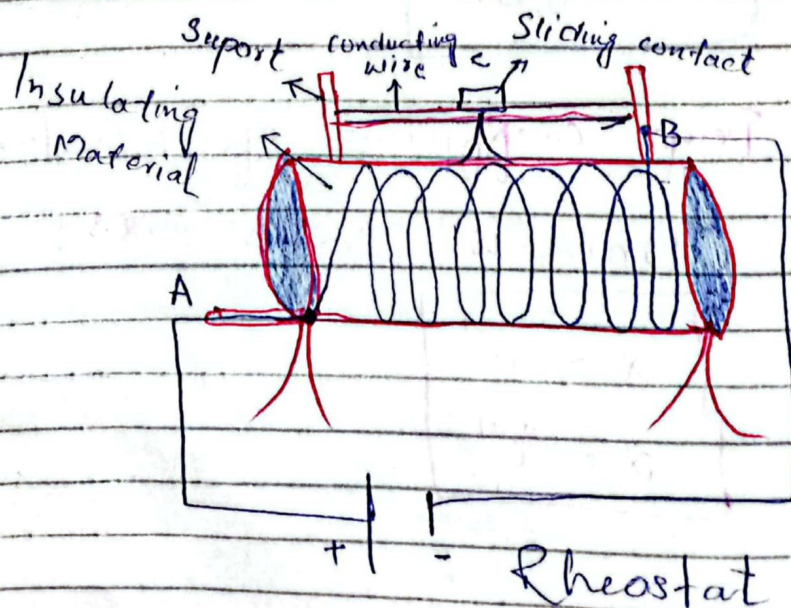
A device by which we can vary the resistance in a circuit is called Rheostat.



Resistance is must for a circuit.


* Rheostat is a Current Controlling Device.

* Rheostat:-

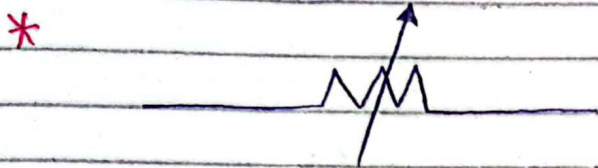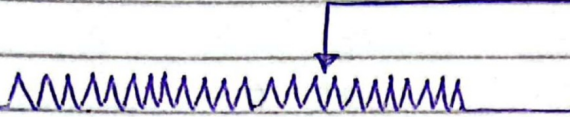

⊗ (II) potential divider:-

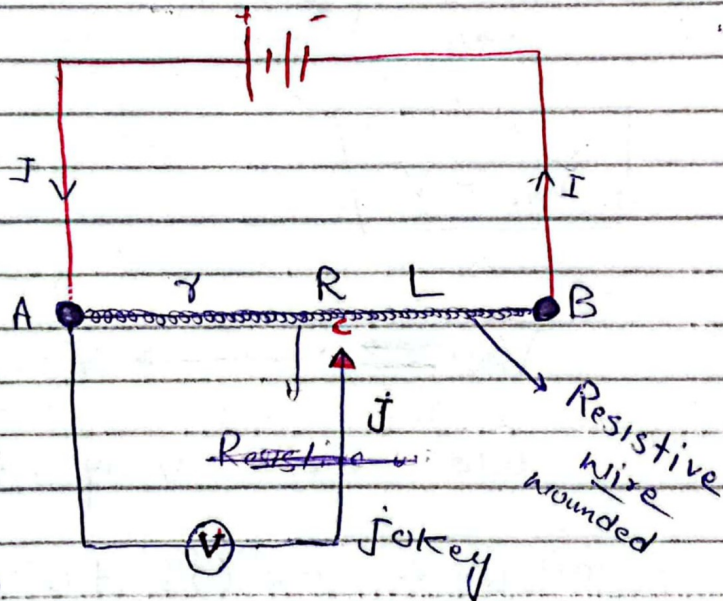A special type of circuit from which we can tap any potential difference from a known P.D or voltage.



$$V_{AC} = Ix \quad \text{--- (i)}$$

$$V_{AB} = IR$$

$$I = \frac{V}{R} \quad \text{--- (ii)}$$

$$V = IR$$

$$I = \text{constant}$$

$$V \propto R \propto L$$

$$V \propto L$$

$$V = IR$$

$$I = \frac{V}{R}$$

$$V_{Ac} = \left(\frac{V}{R}\right) R$$

$$V_{Ac} = \frac{R}{R} (V)$$

$$V_{Ac} = \left(\frac{V}{R}\right) r$$

$$V_{Ac} = V \left(\frac{r}{R}\right) \text{ --- (iii)}$$

When $r = 0$ at A.

$$V_{Ac} = 0$$

When $r = R$ at B.

$$V_{Ac} = V \left(\frac{R}{R}\right)$$

\downarrow
B

$$V_{Ac} = V$$

$$V_{Ac} \Rightarrow 0 \longrightarrow V$$

We can vary (V) from minimum i.e (0) to maximum i.e (V) by potential divider.

2. Thermistors :- Thermal Resistors

Resistors whose Resistance is markedly changing

with temperature are called Thermistors.

* Thermistors are temperature dependent Resistors.

* Thermistors \rightarrow Temperature Sensitive Resistors
 \rightarrow Temperature Sensors.

* There are two types of thermistors :-

(i) PTCs (Positive temperature coefficient thermistors). $\alpha = +ive$

(ii) NTCs (Negative temperature coefficient thermistors). ($\alpha = -ive$)

$$\alpha = \frac{\Delta R}{R_1 \Delta T}$$


$$\alpha = \frac{R_2 - R_1}{R_1 \Delta T}$$

When $R_2 > R_1$ (Resistance Increases)

$$\alpha = +ive$$

When $R_2 < R_1$ $\alpha = -ive$

$$E = \frac{W}{q}$$

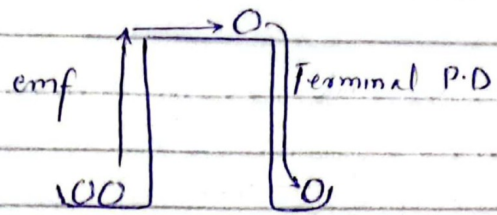

* The phenomena will occur when a source convert non-electrical energy to electrical energy.

Source of emf:-

Non E. energy \longrightarrow E. Energy.

Example:-

- (i) Battery $C.E \longrightarrow E.E$
- (ii) Generator $M.E \longrightarrow E.E$
- (iii) Thermocouple $H.E \longrightarrow E.E$
- (iv) Solar Cell $L.E \longrightarrow E.E$

^{non.} Source $\rightarrow E \rightarrow$ Electrical.

Circuit \rightarrow Electrical \rightarrow Non-electrical.....

Internal Resistance of a Source:-

$$E = IR$$

$$I = \frac{E}{R} \text{ --- (i)}$$



Example:-

$$E = 12V$$

$$R = 4\Omega$$

$$I = \frac{12}{4}$$

$$I = 3A$$

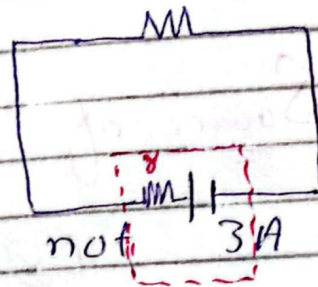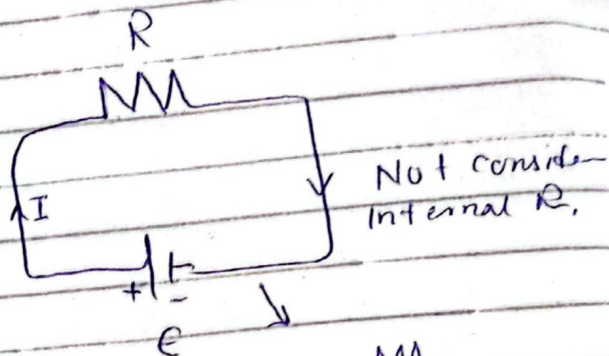

practically current is not 3A

bcz source also has internal resistance. The net current will be less than theoretical.

* We can write eq (i):

$$I = \frac{E}{r+R} \text{ --- (ii)}$$

So I will decrease.

$$E = I(r+R)$$

$$E = Ir + IR$$

$$E = V_{in} + V_{ext} \text{ --- (iii)}$$

Emf = Internal p.d + External p.d

The total strength (voltage) of a source is called emf.

When ~~charging~~


emf increases as we charge the battery and at last it became equal to terminal potential difference when the battery is fully charged...

17 Oct, 2017:

Electric power and power dissipated in Resistors:-

"The power supplied by source"

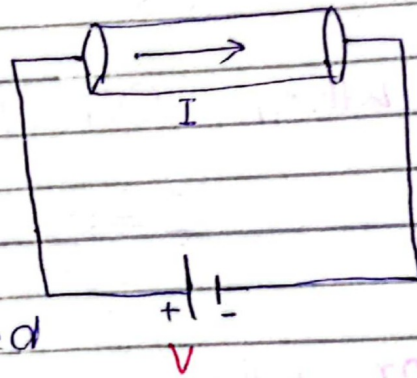The ^{Electric} energy per unit ~~charge~~ time supplied



by a source to a circuit is called electric power.

$$E.P = \frac{E \cdot E}{t}$$

The conversion of electrical energy

into non-electrical energy in a circuit is called energy dissipated.

Electric power: Power Dissipated; the Conversion of electric energy per unit time into non-electrical energy in a circuit is called power dissipated.

$$P = \frac{W}{t} \quad \text{--- (i)}$$

$$V = \frac{W}{q}$$

$$W = qV$$

$$W = qV \quad \text{--- (ii)}$$

put (ii) in (i).

$$P = \frac{Q}{t} (V)$$

$$\frac{Q}{t} = I$$

$$P = IV \quad \text{--- (iii)}$$

Electric power ~~dissipated~~

As, $V = IR$

$$P = I^2 R \quad \text{--- (iv)}$$


Power dissipated in Resistor.

The conversion of electrical energy \rightarrow heat energy \rightarrow per unit time \rightarrow power dissipated in Resistor.

As $I = \frac{V}{R}$

$$P = \frac{V^2}{R} (R)$$
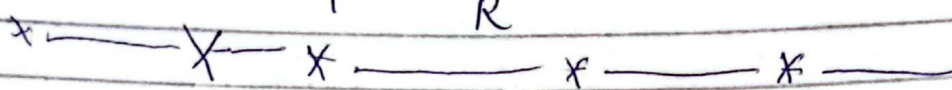
$$P = \frac{V^2}{R} \quad \text{--- (v)}$$



∴ $W = Pt$
Energy dissipated :-

$$W = IVt \quad \text{--- (vi)}$$

$$W = I^2 R t \quad \text{--- (vii)}$$

$$W = \frac{V^2}{R} t \quad \text{--- (viii)}$$

energy dissipated in Resistor

$W = I^2 R t \Rightarrow$ Also called joule's heating law..

Unit :- $P = \frac{W}{t}$

$$1 \text{ Watt} = 1 \frac{\text{J}}{\text{s}}$$

$$1 \text{ Kw} = 10^3 \text{ w}$$

$$1 \text{ Mw} = 10^6 \text{ w}$$

$$1 \text{ H.P} = 746 \text{ w}$$

Commercial Unit of Power \rightarrow Basically energy

$$1 \text{ kWh} = (10^3 \text{ w}) (3600 \text{ sec})$$

$$= 36 \times 10^5 \text{ w.s}$$

$$1 \text{ kWh} \text{ Energ} = 3.6 \times 10^6 \text{ J}$$

$$P = \frac{W}{t}$$

$$W = P \cdot t$$


Maximum power out:-
 "Maximum out put power".

$$P_{out} = I^2 R \quad \text{--- (i)}$$

Net emf \rightarrow

$$E = I r + I R$$

$$E = I (r + R)$$

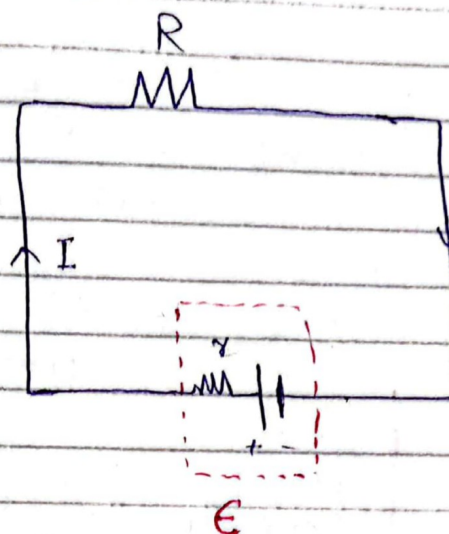

$$I = \frac{E}{r + R} \quad \text{--- (ii)}$$

put in (i).

$$P_{out} = \left(\frac{E}{r + R} \right)^2 R$$

$$P_{out} = \frac{E^2}{(r + R)^2} R \quad \text{--- (iii)}$$

It is minimum \rightarrow power out will be maximum.

$$(r + R)^2 = r^2 + R^2 + 2rR$$

$$(r + R)^2 = r^2 + R^2 - 2rR + 2rR + 2rR \quad \left(\begin{array}{l} \text{Add } 2rR \text{ and} \\ - 2rR \end{array} \right)$$

$$(r + R)^2 = (r - R)^2 + 4rR \quad \text{--- (iv)}$$

eq (iii) \Rightarrow

$$P_{out} = \frac{E^2}{(r - R)^2 + 4rR} R \quad \text{--- (v)}$$

is clear that:

It shows that:

When Internal Resistance = External Resistance
 $r = R$ $P_{out} = (P_{out})_{max}$

$$(P_{out})_{max} = \frac{e^2}{(R-r)^2 + 4Rr} (R)$$

$$(P_{out})_{max} = \frac{e^2}{4R}$$

$$(P_{out})_{max} = \frac{e^2}{4R}$$

This is a theoretical approach,
practically it is not possible

i.e. $r = R$...

P.b #1 Given data:

$$V = 12.8$$

$$I = 3.2A$$

$$\Delta t = 5m$$

$$\Delta t = 300s$$

(i) $R = ?$ $V = IR$

(ii) $\Delta Q = ?$ $I = \frac{\Delta Q}{\Delta t}$

P.b #2: Data:-

$$R_1 = 0.125$$

$$t_1 = 20^\circ$$

$$t_2 = 85^\circ$$

~~Req~~ $\Delta t = t_2 - t_1 = 85 - 20 = 65^\circ$

~~Req~~ $\alpha = -0.0005$

Calculate: $R_2 = ?$

~~or~~ AR

$$R_2 = R_1(1 + \alpha \Delta t)$$

P.b #3 :-

$$L = 10 \text{ m}$$

$$D = 2 \text{ mm}$$

$$\phi = 1 \text{ mm}$$

$$R_{eq} \sim \rho = 2.63 \times 10^{-2} \text{ } \Omega \cdot \text{m.}$$

$$R = ?$$


$$R = \frac{\rho L}{A}$$

$$R = \frac{2.63 \times 10^{-2} \times 10}{\pi r^2}$$

19 Oct, 2017

Kirchoff's Law :-

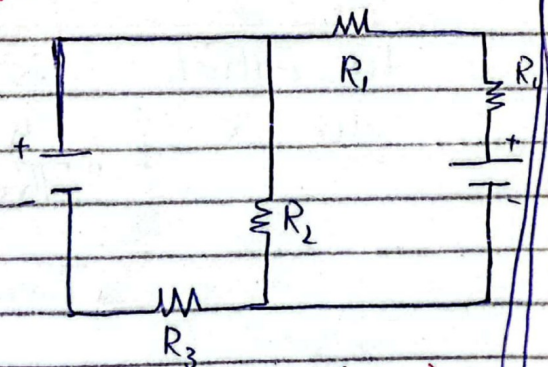We can't decide
that resistors are
in parallel or
series.



Complex Circuits

Dated: 18 Oct, 2017

Thermocouple:-


Any arrangement of two different metals

in which thermoelectric current flows due to the temperature gradient (difference) between

its hot and cold junctions is called thermocouple.

Hot \longrightarrow Cold

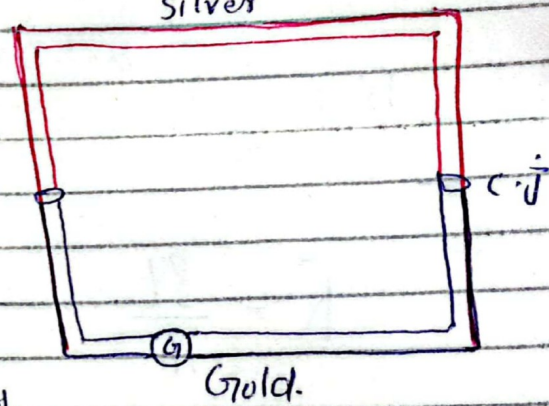* In 1821, (Seebeck) discovered that Heat energy can be converted into electrical energy.



* This conversion is called Seebeck effect. Heat Energy \longrightarrow Gain by $e_s \longrightarrow e_s$ also move from H-j \longrightarrow Cold junction \longrightarrow thermoelectric current.

* The potential difference (emf) due to which e_s move from H-j to C-j is called "Thermoelectric emf"
 \downarrow
Thermoelectric Current.

El.

$$\text{Electronic Density} = \frac{\text{Nu of } \bar{e}s^{\text{free}}}{\text{Volume}}$$


In thermoelectric Current ↓
* $\bar{e}s$ move from High electron density metal to Low electron density.

$$E_T = \alpha T + \frac{1}{2} \beta T^2$$

$\alpha, \beta \Rightarrow$ Thermoelectric co-efficient
The change in Thermoelectric emf

with rise in temperature is called Thermoelectric co-efficient. (α, β)

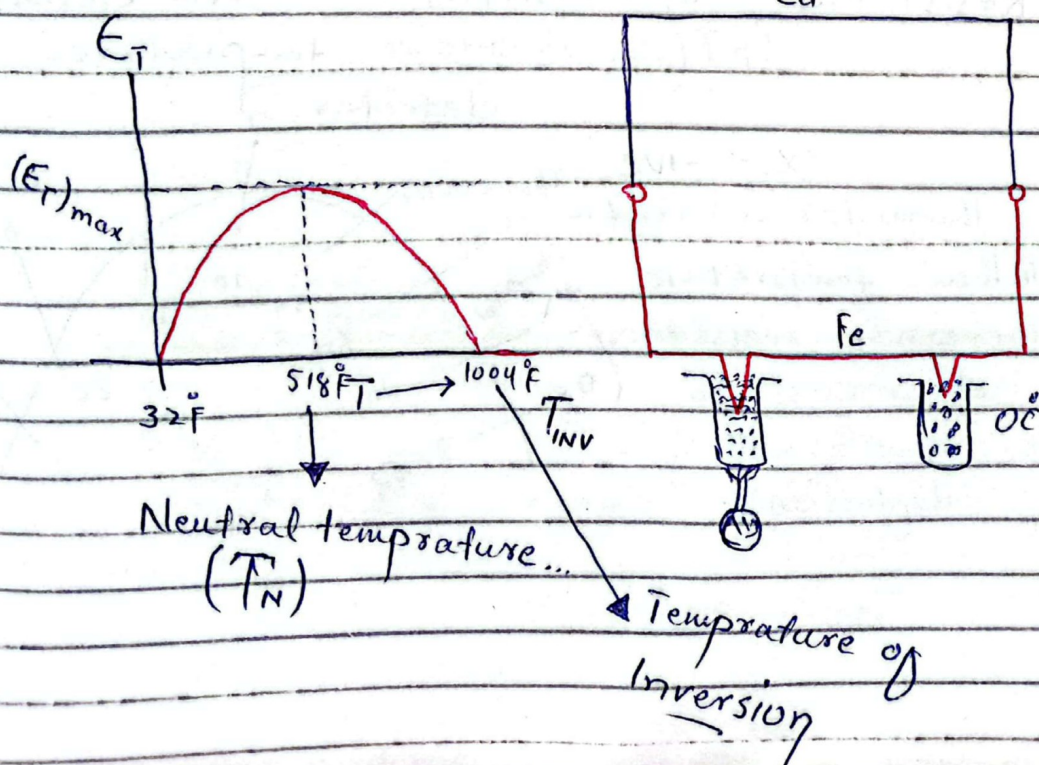Variation in thermoelectric emf with Temperature:-



At " T_{INV} " \rightarrow Electrons gain enough heat

which are randomized \rightarrow which increases resistance \rightarrow So the emp become zero at T_{INV} and the state of Thermocouple is Inversed...


"Thermoelectric effect is reversible when the order of junction is changed..."

Resistance Thermometers:-


They utilize the resistance property of matter to measure

the temperature.

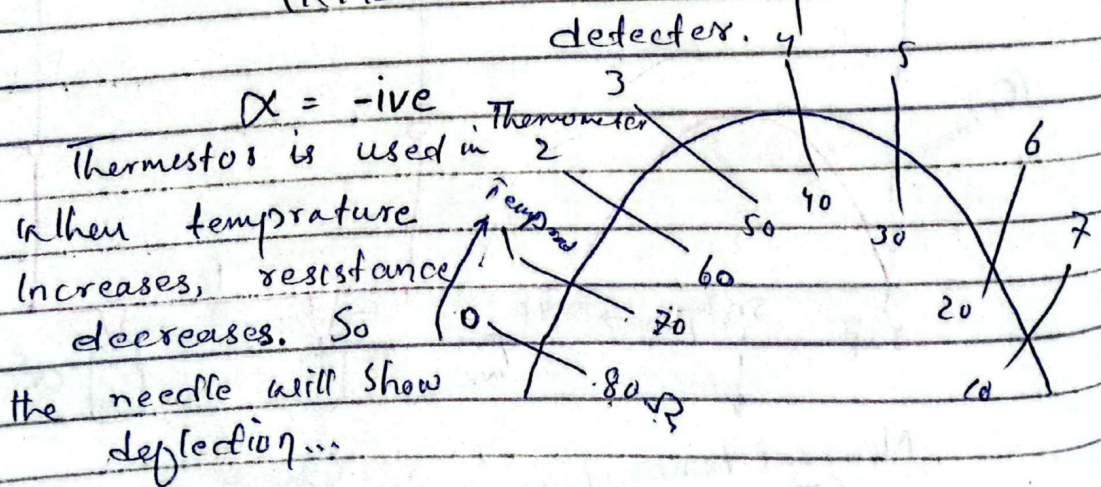* Resistance Thermometers are called (RTDs). \rightarrow Resistance temperature



Numerical # 10

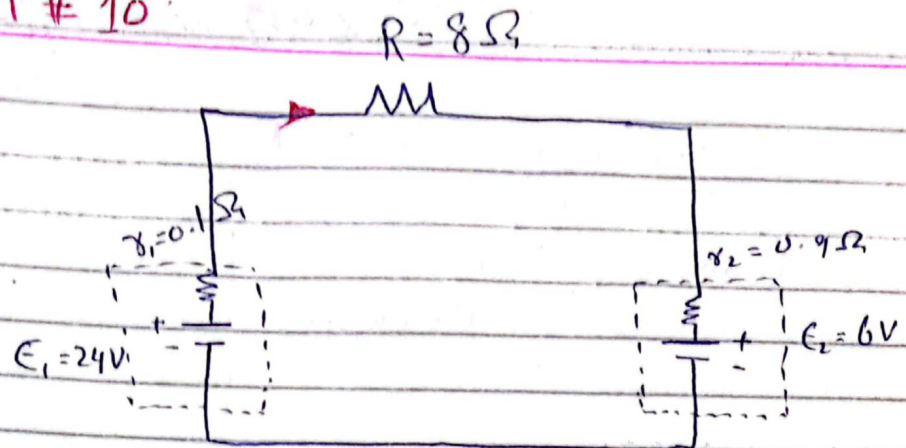

$$R = 8\Omega$$

$$r_1 = 0.1\Omega$$

$$r_2 = 0.9\Omega$$

$$E_1 = 24V$$

$$E_2 = 6V$$

$$V_1 = ?$$

$$V_2 = ?$$

Now $E_1 = I r_1 + IR$

$$E_1 = I r_1 + V_{t1} \quad \text{--- (1)}$$

$$V_{t1} = E_1 - I r_1$$

$$V = E_1 - E_2$$

$$V = 18V$$

$$R_e = r_1 + R + r_2$$

$$R_e = 0.1\Omega + 8\Omega + 0.9\Omega$$

$$R_e = 9\Omega$$

$$V = IR$$


$$V_{t2} = E_2 - (-I r_2) \quad \text{For Second Cell}$$

19 OCT 2017

Kirchoff's Law:-

There are two law's of Kirchoff:

① Kirchoff's Current Law (KCL):-

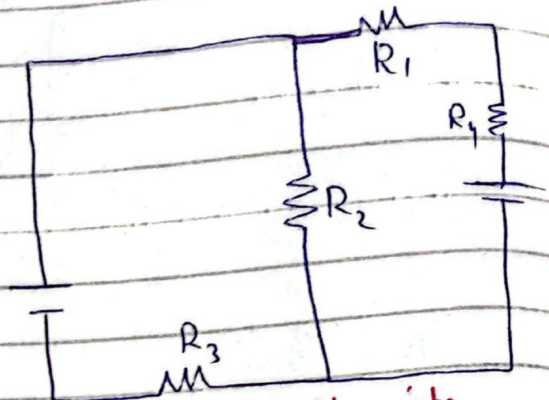


This Law States that "The ^{Complex} algebraic

Sum of all the Current at a junction in a circuit

is equal to zero".

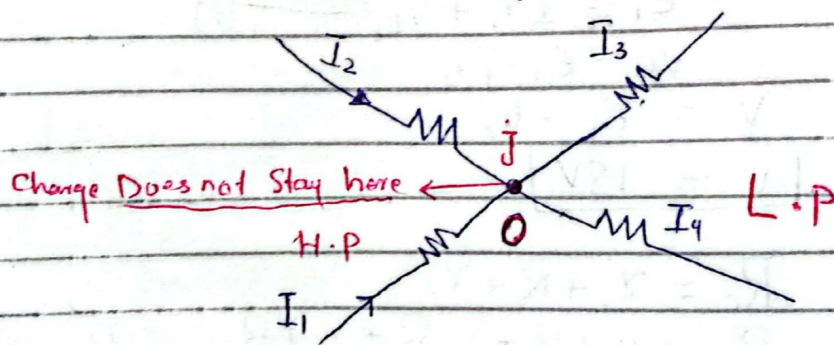* Algebraic Sum:- In which +ive and -ive are not neglected...



junction:- Current enter and leave the Σ Resistor

Conventions:-

① Current entering the junction are considered to be positive.

② Current leaving the junction is -ive.

$$\sum i = 0$$

$$I_1 + I_2 + (-I_3) + (-I_4) = 0$$

$$I_1 + I_2 - I_3 - I_4 = 0 \text{ (Algebraic Sum)...}$$

$$I_1 + I_2 = I_3 + I_4$$

$$\boxed{\sum_E I = \sum_L I}$$

Sum of current entering the junction =
Sum of current leaving the junction...

This law means that:

$$\frac{\Delta Q_E}{\Delta t} = \frac{\Delta Q_L}{\Delta t}$$

$$\boxed{\Delta Q_E = \Delta Q_L}$$

Shows that:

① charge does not stay on the junction.

② KCL is manifestation of the law of conservation of charge.


② Kirchoff's Voltage Law :- (KVL)

This Law States that

"The algebraic Sum of all the Voltage changes ^{in a} around

a Loop in a Circuit is equal to zero.

$$\sum V = 0$$

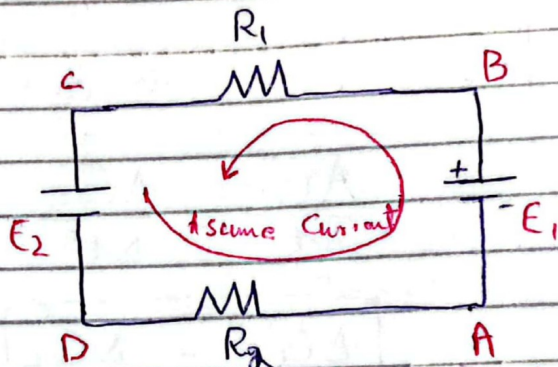

ABCD is a Loop

Conventions:-

- ① Inside the Source when we go from -ive to positive terminal E is taken to be positive, $E = +ve$
- ② When we go in the Source we from +ive to -ive take E negative, $E = -ive$.

③ When we go Along the

}

direction of assumed current.
IR Drop = -ive

(iv) In opposite direction of
assumed current,
IR Drop = +ive

Applying KVL to loop ABCDA:

$$\sum V = 0$$

$$E_1 - IR_1 - E_2 - IR_2 = 0$$

$$E_1 - E_2 = IR_1 + IR_2$$

$$\sum E = \sum IR$$

Algebraic Sum of all emf's
= Algebraic Sum of all IR drops..

$$\cancel{W_s} = \cancel{W_r}$$

$$W_s = W_r$$

| Energy Supplied = Energy dissipated

KVL is a manifestation of

the Law of Conservation of Energy...

Numerical #9:-


Data:-

$$E_1 = 6V$$

$$E_2 = 10V$$

$$R_1 = 1\Omega$$

$$R_2 = 2\Omega$$

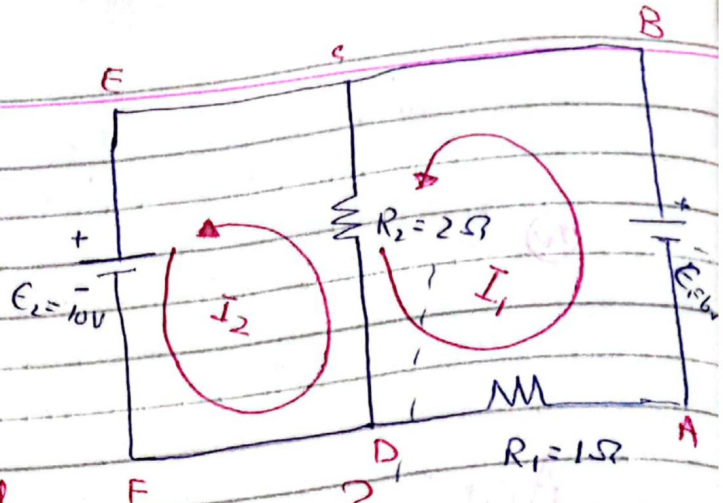

Calculate the Current passing through R_1 and $R_2 = ?$

(i) Applying KVL to loop ABCDA:

$$E_1 - I_1 R_2 + I_2 R_2 - I_1 R_1 = 0$$

$$6V - 2I_1 + 2I_2 - I_1 = 0$$

$$6 - 3I_1 + 2I_2 = 0 \quad \text{--- (i)}$$

(ii) Applying KVL to loop EFDCE:

$$-E_2 - I_2 R_2 + I_1 R_2 = 0$$

$$-10 - 2I_2 + 2I_1 = 0 \quad \text{--- (ii)}$$

Adding (i) and (ii):

$$-10 + 2I_1 - 2I_1 = 0$$

$$6 - 3I_1 + 2I_2 = 0$$

$$-4 - I_1 = 0$$

$$\boxed{I_1 = -4A}$$

put $I_1 = -4A$ in eq (i)

$$6 - 3(-4) + 2(I_2) = 0$$

$$I_2 = -9A$$


Current passing through $R_1 = I_1 = -4A$

Current passing through $R_2 = I_2 = I_2 - I_1$
 $= -9A + 4A$
 $= -5A$

20 Oct, 2017

Wheatstone Bridge Scientist \downarrow Circuit ~~Current~~ :-

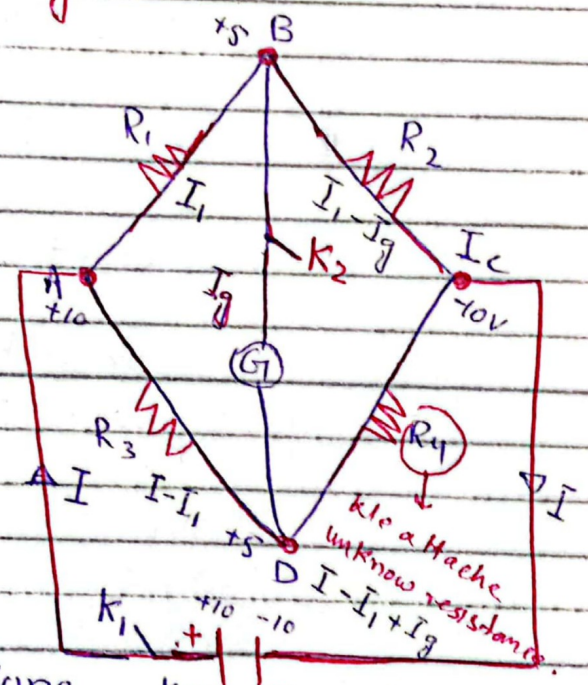It is a special type of electric circuit by which we determine the resistance of an unknown resistor is called wheatstone bridge circuit.




Potential Differences across R_1, R_2, R_3 and R_4 :

$$V_1 = I_1 R_1 \quad \text{--- (i)}$$

$$V_2 = (I_1 - I_g) R_2 \quad \text{--- (ii)}$$
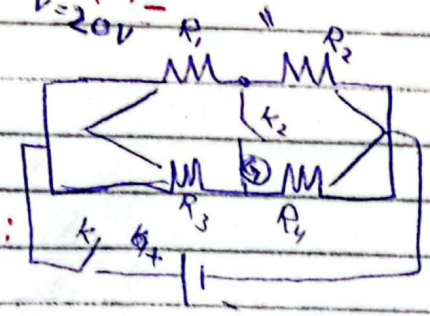
$$V_3 = (I - I_1) R_3 \quad \text{--- (iii)}$$



$$V_4 = (I - I_1 + I_g) R_4 \text{ --- (IV)}$$

When point B and D become at

the same potential: Then potential difference across the galvanometre

will be zero.

$\therefore I_g = 0$ NO current passing...

$$\text{eq (I)} \Rightarrow V_2 = I_1 R_2 \text{ --- (5) } I_g = 0$$

$$\text{eq (II)} \Rightarrow V_4 = (I - I_1) R_4 \text{ --- (6)}$$

$$V_1 = V_3 \text{ --- (7)}$$

$$V_2 = V_4 \text{ --- (8)}$$

put values in (7) and (8)!

$$I_1 R_1 = (I - I_1) R_3 \text{ --- (9)}$$

$$I_1 R_2 = (I - I_1) R_4 \text{ --- (10)}$$

Dividing (9) by (10)!

$$\frac{I_1 R_1}{I_1 R_2} = \frac{(I - I_1) R_3}{(I - I_1) R_4}$$

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

$$R_1 R_4 = R_2 R_3$$

$$R_4 = \frac{R_2 R_3}{R_1}$$

$$X = \frac{QR}{P}$$

$$Q = R_2, P = R_1$$

$$R = R_3$$

sol. \rightarrow Potential divider

potentiometer :-

A device by which



we measure the

emf of an unknown Cell.

21 OCT 2017

$$V_{AC} = I \gamma_x \quad \text{--- (i)}$$

$$V = IR$$


$$I = \frac{V}{R} \quad \text{--- (ii)}$$

put in (i) :

$$V_{AC} = \left(\frac{V}{R}\right) \gamma_x$$

~~$$V_{AC} = \frac{\gamma_x}{R} V$$~~
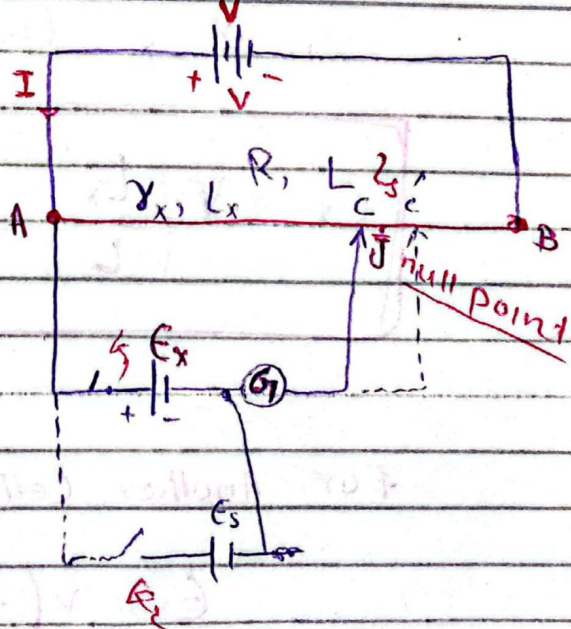
$$V_{AC} = \left(\frac{\gamma_x}{R}\right) V \quad \text{--- (iii)}$$



As,

$$R \propto L$$
$$R = kL \text{ --- (iv)}$$

$$r_x \propto L_x$$

$$r_x = kL_x \text{ --- (v)}$$

Dividing (v) by (iv):

$$\frac{r_x}{R} = \frac{kL_x}{kL} \text{ --- (vi)}$$

$$\frac{r_x}{R} = \frac{L_x}{L}$$

put eq (vi) in (iii):

$$V_{AC} = V \left(\frac{L_x}{L} \right)$$

$V_{AC} = \epsilon_x$ (when ϕ voltage across AC is equal to emf)

$$\epsilon_x = V \left(\frac{L_x}{L} \right) \text{ --- (vii)}$$



For Another Cell:-

$$\epsilon_s = V \left(\frac{L_s}{L} \right) \text{ --- (viii)}$$

Dividing eq (viii) by (vii):

$V = \frac{E_s}{L} \times L$
 $V = \frac{E_x}{L} \times L$
 $V = \frac{E_s}{L} \times L$

$$\frac{E_s}{E_x} = \frac{V \left(\frac{L_s}{L} \right)}{V \left(\frac{L_x}{L} \right)}$$

$$\frac{E_s}{E_x} = \cancel{V} \left(\frac{L_s}{\cancel{L}} \right) \times \frac{1}{\cancel{V}} \left(\frac{L}{L_x} \right)$$

$$\boxed{\frac{E_s}{E_x} = \frac{L_s}{L_x}}$$

comparison of emf of two cells by potentiometer...

emf of source \propto Length

Example: $\frac{E_s}{E_x} = 2$

① E_x

E_s is double of E_x .

$\frac{E_s}{E_x} = \frac{1}{2}$ E_s is half of E_x ...