

\* CH #17 \* 05 Dec 2017

## Electronics:

The study of the Behaviour of  $e^-$  in electric circuits.

(I) Semiconductors:-

$\rho \sim 10^{-4} \Omega \cdot m \rightarrow$  Conductors

$\rho \sim 10^8 \Omega \cdot m \rightarrow$  Insulators

$\rho \sim 10^4 \Omega \cdot m \rightarrow$  S.Cs. (Semiconductors)

-: PERIODIC TABLE :-

(i) Metals  $\rightarrow$  Conductors (Free  $e^-$ )

(ii) Non-Metals  $\rightarrow$  Insulators (No free  $e^-$ )


Pure (iii) Metalloid (Ge, Si)  $\rightarrow$  Semi-conductors.

Intrinsic and Extrinsic Semiconductors  
(N-type and P-type Semiconductors)

\* pure Semiconductors are called Intrinsic Semiconductors.

\* Bond energy of Germanium (Ge) = 0.72 eV

\* Bond energy of Silicon (Si) = 1.09 eV

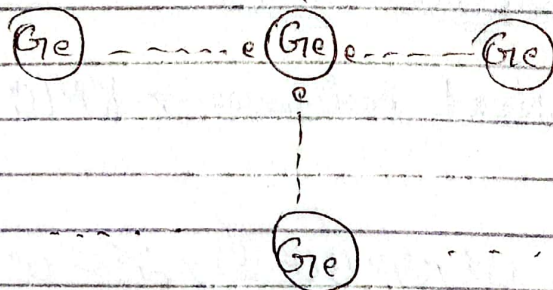

\* In Intrinsic Semiconductors  $e^-$  and


Holes are responsible for conduction.



\* The conduction effect of Semiconductor is less, so we add impurities to them.

\* When impurities are added or doping is done, the conduction level of Semiconductor increases and the Semiconductor is called Extrinsic Semiconductor.

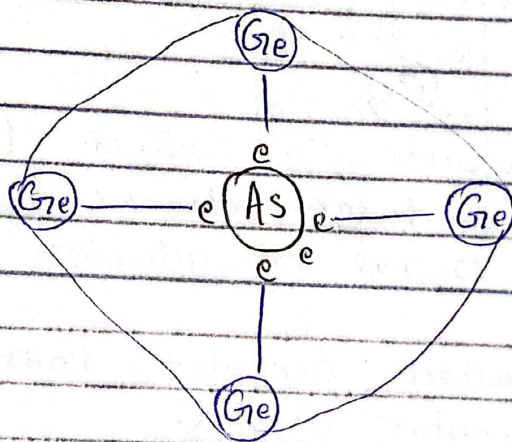Extrinsic Semiconductors are of 2 types:-



\* Impure Semiconductor or Extrinsic Semiconductor or Doped semiconductor.

\* The Arsenic (As) is called Donor Impurity or Donor Dopant.

\* In this case when:


\* One bond is broken, one hole and two  $e^-$  are freed. So on.

\* In these types materials, the  $e^-$  are in majority, so mainly conduction



Occure due to  $\bar{e}$ s.  
Such Materials are called N-type materials.

\* Overall charge = Zero:

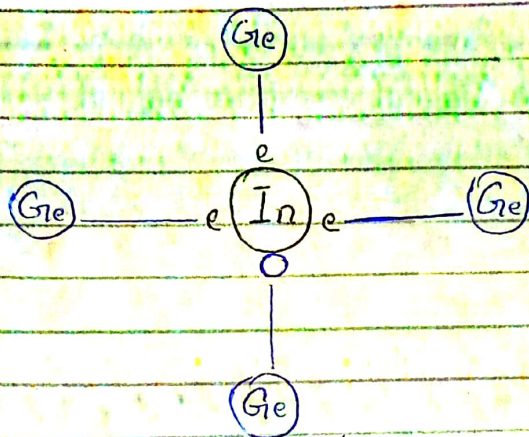

This Material is called Impure Semiconductor (Extrinsic Semiconductor) Doped Semiconductor

\* (In) is called Acceptor Impurity or Acceptor Dopant.

In these materials:

When one Bond is broken one Electron and two holes are Created and so on.

\* In these materials the Conduction Occure mainly due to Holes therefore these materials are called P-type Materials.




06 NOV 2017

## PN-junction or Semiconducting Diode:-

When a P-type material is pressed with N-type material under

A particular fabrication process is called PN-junction or


Semi-conducting diode.

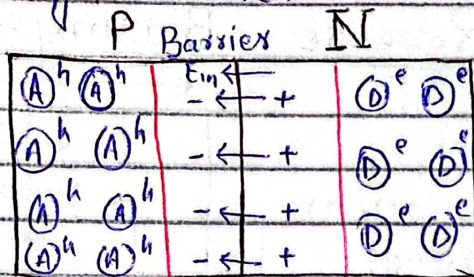

1. At beginning a small current is passes which is called diffusion current.

2. When a Barrier potential is developed the current stops.

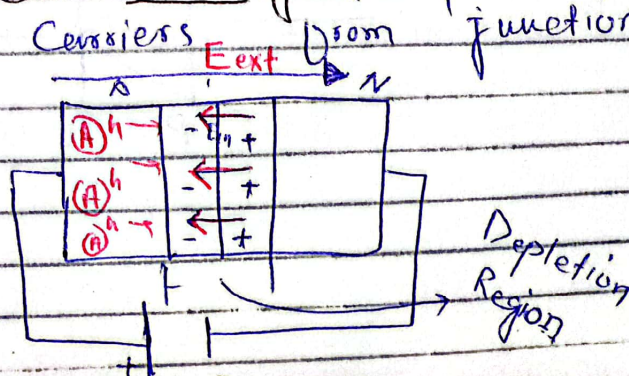1. Forward Biasing  $\rightarrow$  (to pass charge carriers from junction).






\* In case of Forward Biasing  
 the thickness of Depletion region  
 Decreases. I.e Current passes  
 Increases.

Diode  
 Two ↓  
 Holes → passage → Path

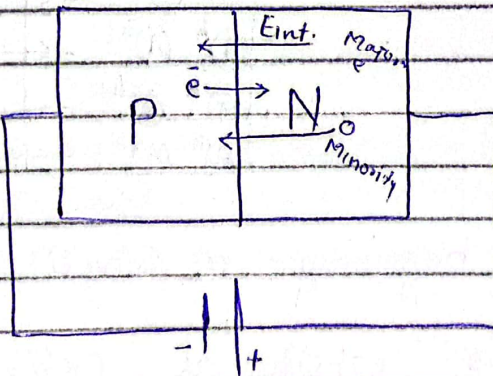
2. Reverse Biasing:-

(Minority  
 charge carriers  
 are passing)  
 (Try to Understand)




\* In this case the Barrier will increase  
 and hence current flow decreases.

Electronic Symbol for Diode:-

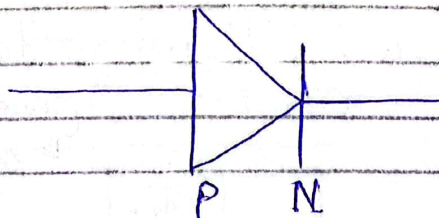


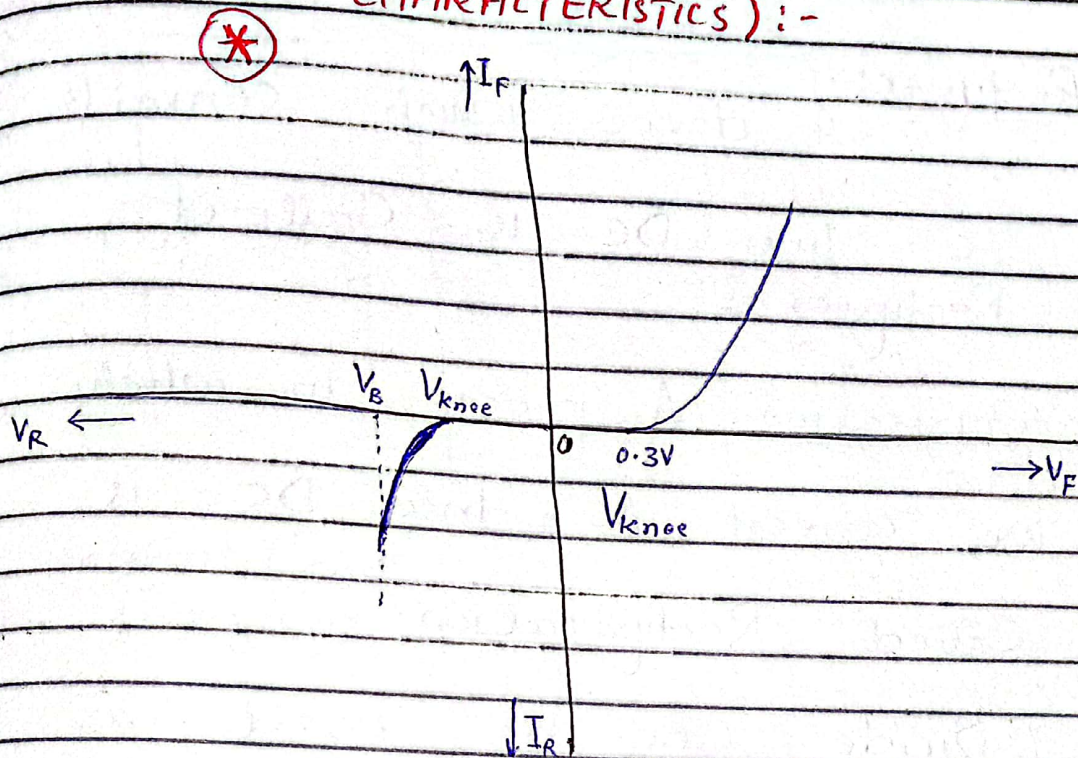
## CHARACTERISTICS OF Diode (I-V CHARACTERISTICS):-



\* The Barrier potential of Ge Diode = 0.3V

\* The Barrier potential of Si Diode =

### 1. Avalanch Break Down ( $V_B$ ).

Maximum  $e^-$ s and holes are moving in their respective direction.

\* At Avalanch Break Down the current become maximum and Break Down take place...



07 Dec 2017

## Diode As a Rectifier:-


Rectifier:-

A device which converts AC into DC is called Rectifier.

Rectification: A process in which we convert AC into DC is called Rectification.

\* Diode can be used as a rectifier.


### 1. Half wave Rectifier:-

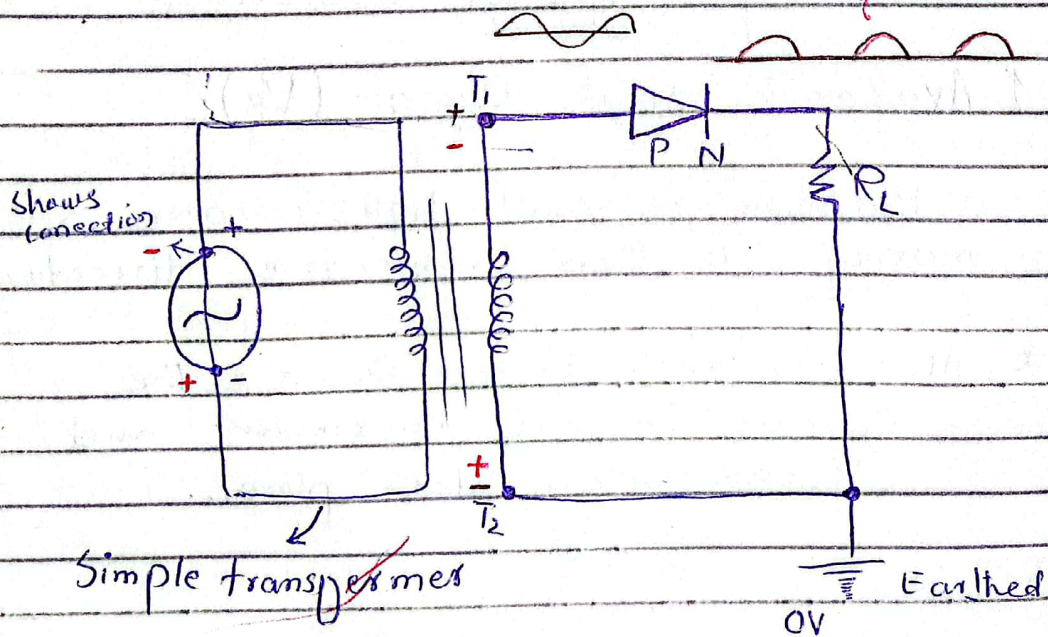



## Centre tap design

### 2. Full Wave Rectifier :-

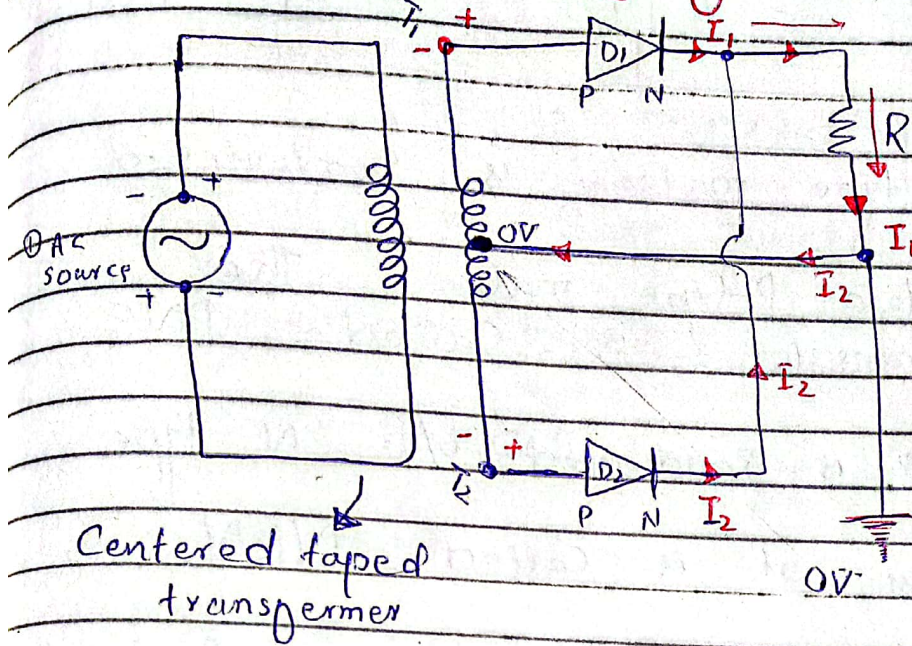

\* 0V  $\Rightarrow$  Ground or Common potential.

\* Centered tapped transformer is used in full wave rectifier to complete the circuit.


\* 08 Dec 2017 \*

Exam Quest
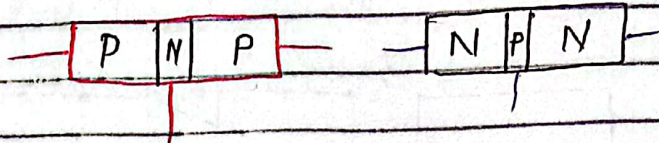
### Transistor :-

When diodes are pressed together back to back in such away that the centre portion is made thinner, the device form is called Transistor.





\* If N-type material is sandwiched


b/w two P-type material then transistor is called PNP

\* If P is sandwiched b/w N-type

then it is called NPN.

\* Diode is a two terminal semi-conducting device. While a transistor

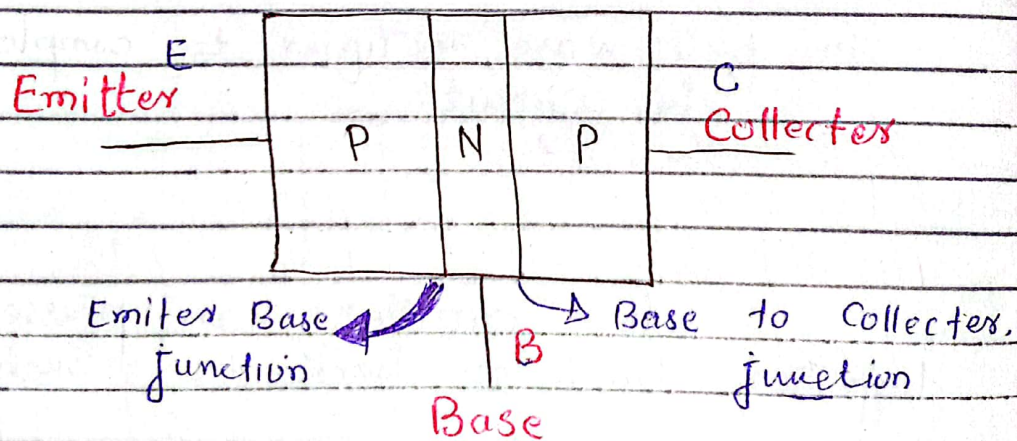is three terminal semi-conducting device...



1. Emitter:- The side which is highly/Heavily Doped.

2. Base:- Central part. It is very



Lightly Doped

### 3. Collector:-

It is moderately doped.


\* Emitter to Base junction is

forward Biase

\* Base to Collector junction is

reversed Biase.

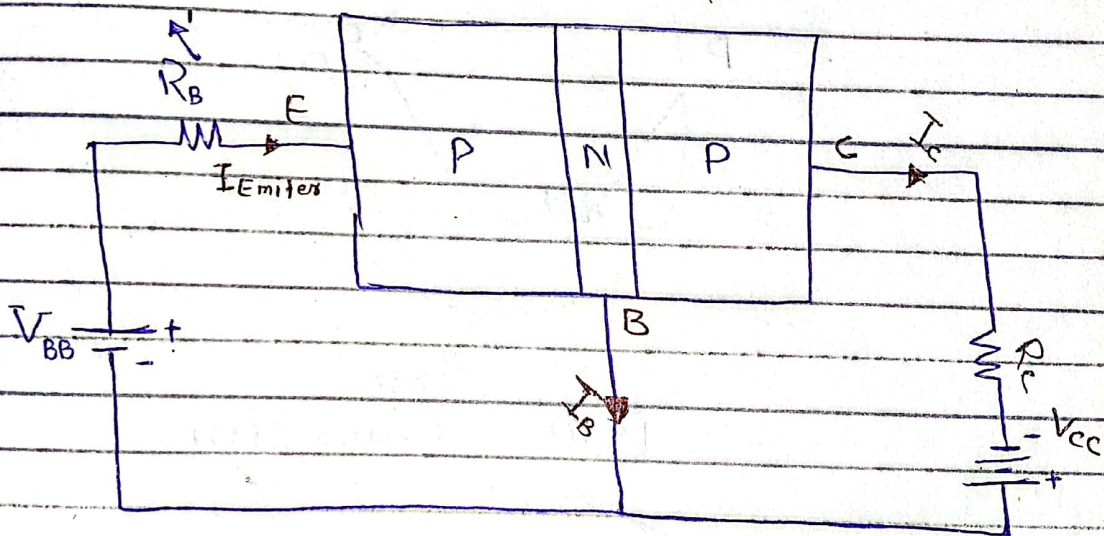\* A resistor ( $R_B$ ) is connected with P-type.



$V_{BB} \Rightarrow$  Forward biasing battery  
In Transistor:-

$$V_{CC} > V_{BB}$$

According to KCL

$$I_E = I_B + I_C \rightarrow \text{Basic equation for}$$

Transistor.





Transistor can be attached in a circuit in 3 ways:

(I) COMMON BASE CONFIGURATION:-

Configuration of a transistor in a circuit which such that Base is common in both input and output sides.


Symbol for Transistor:-

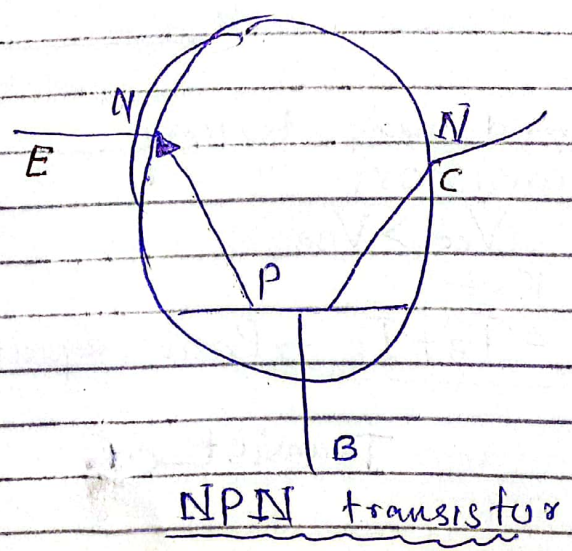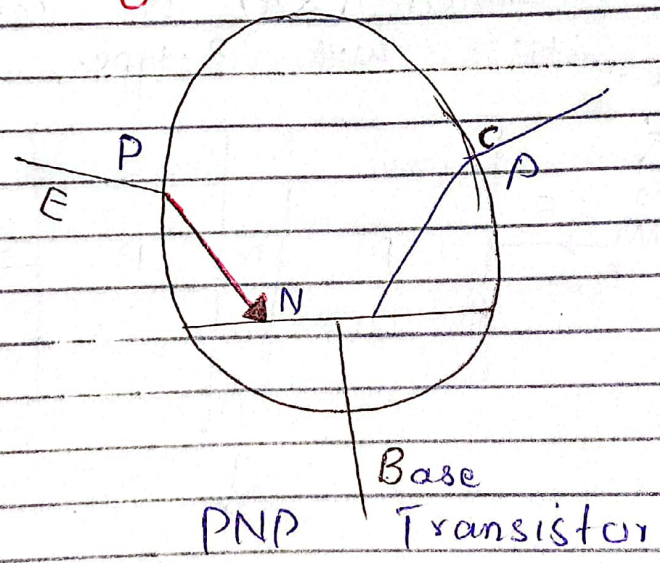



10 Dec 2017


### Common - Emitter Configuration:-

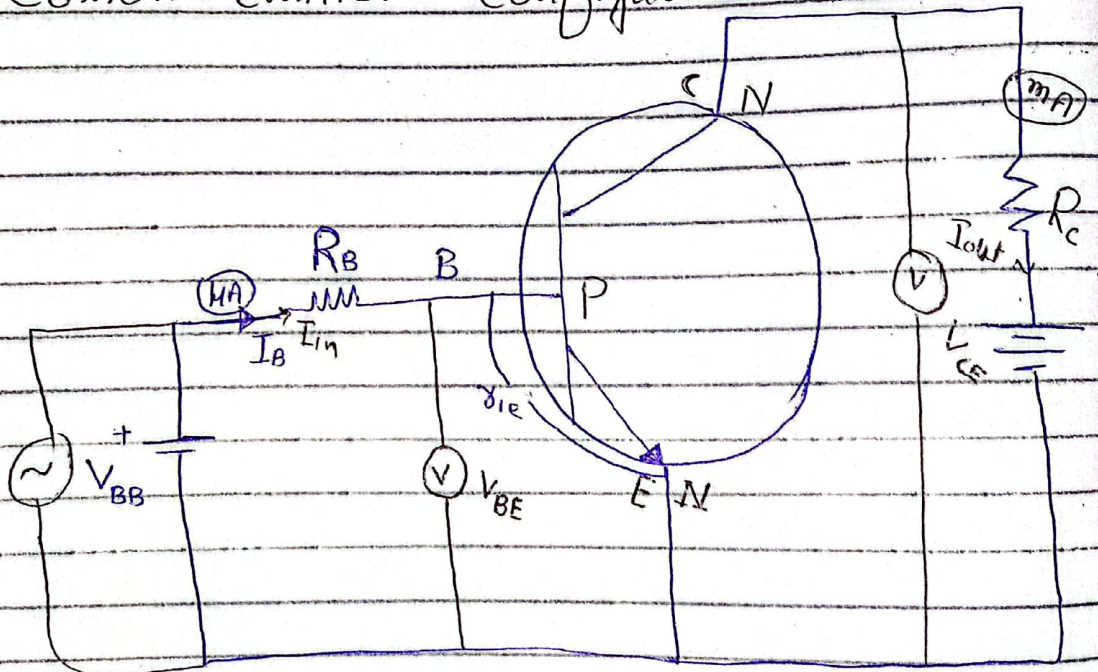

Output characteristics:-
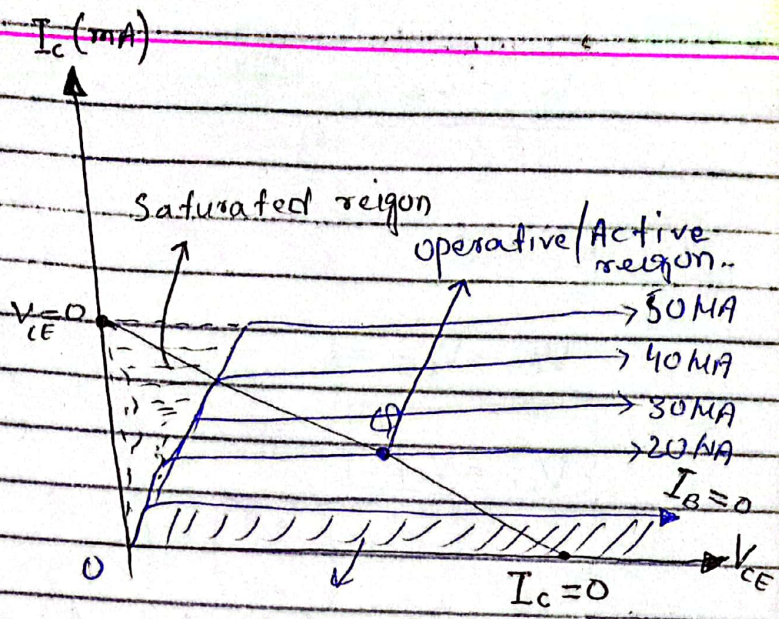
$$I_C \longrightarrow V_{CE} \quad (I_B = \text{constant})$$





\* In cut off region transistor act as  
 up open switch.

\* Saturated region  $\rightarrow$  it act like  
 on switch.

\* Q is operative/Active region  
 In this region transistor Act as  
 Amplifier.

$$V_{cc} = V_c + V_{ce}$$

$$V_{cc} = I_c R_c + V_{ce}$$

$$I_c = \frac{V_{cc} - V_{ce}}{R_c}$$

$$V_{ce} = 0$$

$$I_c = \frac{V_{ce}}{R_c} \text{ (Max)}$$

$$I_c = 0$$



$$\frac{V_{CC} - V_{CE}}{R_C} = 0$$

$$R_C \neq 0$$

So

$$V_{CC} - V_{CE} = 0$$

$$\boxed{V_{CC} = V_{CE}}$$

Transistor As An Amplifier:

A device which convert low AC signals into high AC signals.

$\beta$  = Amplification factor:

$$\beta = \frac{\Delta I_C}{\Delta I_B} \quad \text{--- (1)}$$

$$\Delta I_B = I_{in}$$

$$\Delta I_C = I_{out}$$

$$\beta = \frac{I_{out}}{I_{in}} \quad \text{--- (2)}$$

$$V_{out} = I_{out} R_C$$

$$I_{out} = \frac{V_{out}}{R_C} \quad \text{--- (3)}$$



$$I_{in} = \frac{V_{in}}{r_{ie}} \quad (4)$$

$r_{ie} \rightarrow$  Resistance of NPN ~

put eq (3) and (4) in (2)

$$\beta = \left( \frac{V_{out}}{R_c} \right) \div \left( \frac{V_{in}}{r_{ie}} \right)$$

$$\beta = \left( \frac{V_{out}}{R_c} \right) \times \left( \frac{r_{ie}}{V_{in}} \right)$$

$$\beta = \left( \frac{V_{out}}{V_{in}} \right) \left( \frac{r_{ie}}{R_c} \right)$$

IF  $R_c > r_{ie}$

Then  $V_{out} > V_{in}$

When  $V_{out}$  is greater than  $V_{in}$ , this is called voltage Amplifiers...


11 Dec 2017

### Types of Diode:-

1. LED (Light emitting diode)

A diode which converts electrical energy into Light energy is

called LED.

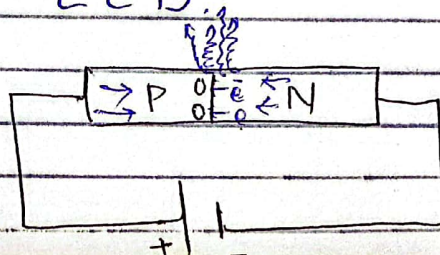




\* LED is Forward Bias.

Symbol for LED:-



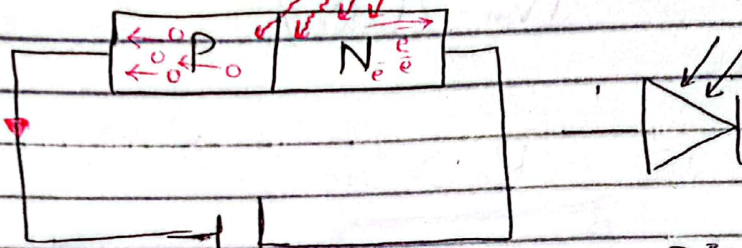2. PhotoDiode:-

A diode which convert light energy into electrical energy is called PhotoDiode.




\* PhotoDiode - + is reversed Bias.

3. Photovoltaic Cell:-

It is a source of voltage or emf.

\* No need of Biasing.

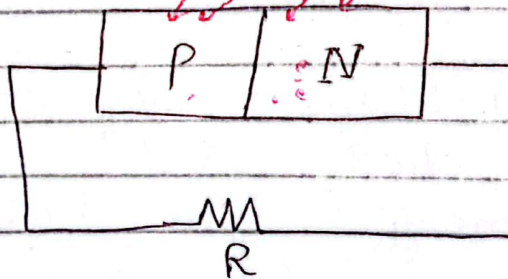



## Relation b/w $\alpha$ and $\beta$ :-

$$\beta = \frac{I_c}{I_B} \quad \text{--- (i)}$$

$$\alpha = \frac{I_c}{I_E} \quad \text{--- (ii)}$$

∴

$$I_E = I_B + I_c$$

$$I_B = I_E - I_c \quad \text{--- (iii)}$$

$$\beta = \frac{I_c}{I_E - I_c} \quad \text{--- (iv)}$$

Dividing the num and denominator of eq (iv) by  $I_E$ :

$$\beta = \frac{\left(\frac{I_c}{I_E}\right)}{\left(\frac{I_E - I_c}{I_E}\right)}$$

$$\beta = \frac{\left(\frac{I_c}{I_E}\right)}{\frac{\frac{I_E}{I_E} - \frac{I_c}{I_E}}{\frac{I_E}{I_E}}}$$

$$\beta = \frac{\left(\frac{I_c}{I_E}\right)}{\left(1 - \frac{I_c}{I_E}\right)} \quad \text{--- (v)}$$

put eq (v) in (i)

$$\beta = \frac{\alpha}{1 - \alpha}$$

$$\alpha = \frac{\beta}{1 + \beta}$$



Saturated region = ON Switch  
Cut off region = OFF Switch

Digital Electronics:-

A system which can be described in two Quantized or discrete states is called Digital electronics.

Low      High

OFF      ON

open      closed

False      True

0      1

\* 0, 1 are called Binary or Boolean numbers.